


CIRCUIT ANALYSIS EXAMPLES

Note Title


10/20/2008

* ALL RESISTORS ARE IDENTICAL FOR THESE EXAMPLES:
FIND V & I FOR SOURCE & EACH LOAD

①

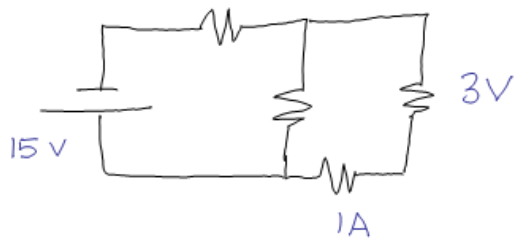

②

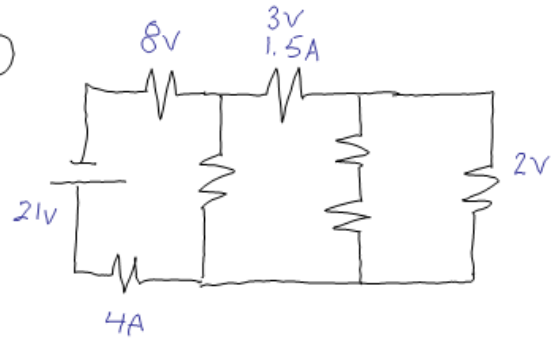

(ALL ANSWERS ON KIRCHHOFF MATH)